

Lecture 4

Counters, Shift Registers & Memory


Prof Peter YK Cheung
Imperial College London

URL: www.ee.ic.ac.uk/pcheung/teaching/EIE2-IAC/
E-mail: p.cheung@imperial.ac.uk

Learning outcomes

- ❖ How to convert from binary to BCD format?
- ❖ How to generate various clock signals with different periods?
- ❖ How to specify shift registers?
- ❖ How to design a Linear Feedback Shift Register (LFSR) that produces pseudo-random binary sequence (PRBS)?
- ❖ How to specify ROM and RAM components?
- ❖ What is in **Lab 2**?


Displaying a binary number as decimal

 

- ◆ In Lab 1 Task 4, you are required to display the counter value as binary coded decimal number instead of hexadecimal. A SystemVerilog component `bin2bcd.sv` is provide.
- ◆ Hex numbers are difficult to interpret. Often we would like to see the binary value displayed as decimal. For that we need to design a combinational circuit to converter from binary to binary-coded decimal. For example, the value `8'hff` or `8'b11111111` is converted to `8'd255` in decimal.

Shift and Add 3 algorithm [1] – shifting operation

- ◆ Let us consider converting hexadecimal number 8'h7C (which is decimal 8'd124)
- ◆ Shift the 8-bit binary number left by 1 bit = multiply number by 2
- ◆ Shifting the number left 8 times = multiply number by 2^8
- ◆ Now truncate the number by dropping the bottom 8 bits = divide number by 2^8
- ◆ So far we have done nothing to the number – it has the same value
- ◆ The idea is that, as we shift the number left into the BCD digit “bins”, we make the necessary adjustment to the hex number so that it conforms to the BCD rule (i.e. falls within 0 to 9, instead of 0 to 15)

 

Shift and Add 3 algorithm [2] – shift left with problem

- ◆ If we take the original 8-bit binary number and shift this three times into the BCD digit positions. After 3 shifts we are still OK, because the **ones digit** has a value of 3 (which is OK as a BCD digit).
- ◆ If we shift again (4th time), the digit now has a value of 7. This is still OK. However, no matter what the next bit it, another shift will make this digit illegal (either as hexadecimal “e” or “f”, both not BCD).
- ◆ In our case, this will be a “f”!

	Hundreth BCD	Tens BCD	Ones BCD	8-bit binary	
Original binary number				0 1 1 1	1 1 0 0
Shift left 1 bit – no problem			0	1 1 1 1	1 0 0 0
Shift left 1 bit - no problem			0 1	1 1 1 1	0 0 0 0
Shift left 1 bit – no problem			0 1 1	1 1 1 0	0 0 0 0
Shift left 1 bit - no problem			0 1 1 1	1 1 0 0	0 0 0 0
Shift left 1 bit – problem, not BCD			1 1 1 1	1 0 0 0	0 0 0 0

Shift and Add 3 algorithm [3] – shift and adjust

- ◆ So on the fourth shift, we detect that the value is $> \text{ or } = 5$, then we adjust this number by adding 3 before the next shift.
- ◆ In that way, after the shift, we move a 1 into the tens BCD digit as shown here.

	Hundreth BCD	Tens BCD	Ones BCD	8-bit binary	
Original binary number				0 1 1 1	1 1 0 0
Shift left 1 bit – no problem			0	1 1 1 1	1 0 0 0
Shift left 1 bit – no problem			0 1	1 1 1 1	0 0 0 0
Shift left 1 bit – no problem			0 1 1	1 1 1 0	0 0 0 0
Shift left 1 bit – no problem			0 1 1 1	1 1 0 0	0 0 0 0
Perform adjustment Before shifting by adding 3			1 0 1 0	1 0 0 0	0 0 0 0
We perform adjustment (if ≥ 5 , add 3) before shift		1	0 1 0 1	1 1 0 0	0 0 0 0

Shift and Add 3 algorithm [4] – full conversion

- ◆ In summary, the basic idea is to shift the binary number left, one bit at a time, into locations reserved for the BCD results.
- ◆ Let us take the example of the binary number 8'h7C. This is being shifted into a 12-bit/3 digital BCD result of 12'd124 as shown below.



	Hundreth BCD	Tens BCD	Ones BCD	8-bit binary	
Original binary number				0 1 1 1	1 1 0 0
Shift left three times no adjust			0 1 1	1 1 1 0	0
Shift left Ones = 7, ≥ 5			0 1 1 1	1 1 0 0	
Add 3			1 0 1 0	1 1 0 0	
Shift left Ones = 5		1	0 1 0 1	1 0 0	
Add 3		1	1 0 0 0	1 0 0	
Shift left 2 times Tens = 6, ≥ 5		1 1 0	0 0 1 0	0	
Add 3		1 0 0 1	0 0 1 0	0	
Shift left BCD value is correct	1	0 0 1 0	0 1 0 0		

SystemVerilog implementation - bin2bcd.sv

```
module bin2bcd (  
    input  logic [7:0]  x,          // value to be converted  
    output logic [11:0] BCD         // BCD digits  
);  
    // Concatenation of input and output  
    logic [19:0] result; // = bit in x + 4 * no of digits  
    integer i;  
  
    always_comb  
    begin  
        result[19:0] = 0;  
        result[7:0] = x; // bottom 8 bits has input value  
  
        for (i=0; i<8; i=i+1) begin  
            // Check if unit digit >= 5  
            if (result[11:8] >= 5)  
                result[11:8] = result[11:8] + 4'd3;  
  
            // Check if ten digit >= 5  
            if (result[15:12] >= 5)  
                result[15:12] = result[15:12] + 4'd3;  
  
            // Shift everything left  
            result = result << 1;  
        end  
  
        // Decode output from result  
        BCD = result[19:8];  
    end  
endmodule
```


A Flexible Timer – clktick.sv

  - ◆ Instead of having a counter that count events, we often want a counter to provide a measure of **time**. We call this a **timer**.
- ◆ Here is a useful **timer** component that uses a clock reference, and produces a pulse lasting for one cycle every $N+1$ clock cycles.
- ◆ If “en” signal is low (not enabled), the clk pulses are ignored.




```
module clktick #(
    parameter WIDTH = 16
)()
    // interface signals
    input  logic      clk,      // clock
    input  logic      rst,      // reset
    input  logic      en,       // enable signal
    input  logic [WIDTH-1:0] N,  // clock divided by N+1
    output logic      tick      // tick output
);

    logic [WIDTH-1:0] count;
```

clktick.sv explained


 
- ◆ “count” is an internal counter with WIDTH bits
- ◆ We use this as a down (instead of up) counter
- ◆ The counter value goes from N to 0, hence there are N+1 clock cycles for each tick pulse



```
always_ff @ (posedge clk)
    if (rst) begin
        tick <= 1'b0;
        count <= N;
    end
    else if (en) begin
        if (count == 0) begin
            tick <= 1'b1;
            count <= N;
        end
        else begin
            tick <= 1'b0;
            count <= count - 1'b1;
        end
    end
endmodule
```



Cascading counters

 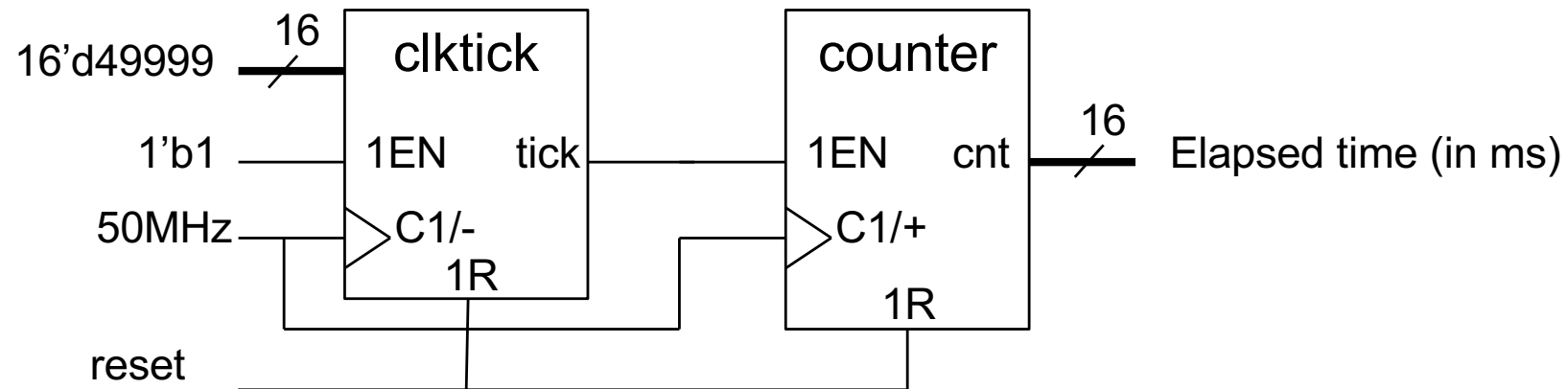- By connecting **clktick** module in series with a counter module, we can produce a counter that counts the number of millisecond elapsed as shown below.



Clock divider (clkdiv.sv)

  
- ◆ Another useful module is a **clock divider circuit**.
- ◆ This produces a **symmetrical** clock output, dividing the input clock frequency by a factor of $2*(K+1)$.



```
module clkdiv #(
    parameter WIDTH = 16
) (
    input logic      clkdiv, // Clock input signal to be divided
    input logic      en,     // enable clk divider when high
    input logic [WIDTH-1:0] K, // half clock period counts K+1 clkdiv cycles
    output logic      clkout // symmetric clock output Fout = Fin / 2*(K+1)
); // End of port list

logic [WIDTH-1:0] count; // internal counter
```

clkdiv.v explained


 


```
initial clkout = 1'b0;           // alternative way to initialise logic
initial count = {WIDTH{1'b0}}    // ... or FF (Good for FPGA designs)

//----- Main Body of the module -----

always_ff @ (posedge clkkin)
    if (en == 1'b1)
        if (count == {WIDTH{1'b0}} begin
            clkout <= ~clkout;           // toggle the clock output
            count <= K; // shift right one bit
        end
        else
            count <= count - 1'b1;
endmodule // End of Module clkdiv
```

  Shift Register specification in SystemVerilog




```

module sreg4 (
    input logic    clk,        // input clock
    input logic    rst,        // reset
    input logic    data_in,    // serial data in
    input logic    data_out    // serial data out
);
    // End of port list

    logic [4:1]    sreg;        // shift register


    always_ff @ (posedge clk)
        if (rst)
            sreg <= 4'b0;
        else begin
            sreg[4] <= sreg[3];
            sreg[3] <= sreg[2];
            sreg[2] <= sreg[1];
            sreg[1] <= data_in;
        end
    assign data_out = sreg[4];
endmodule

```

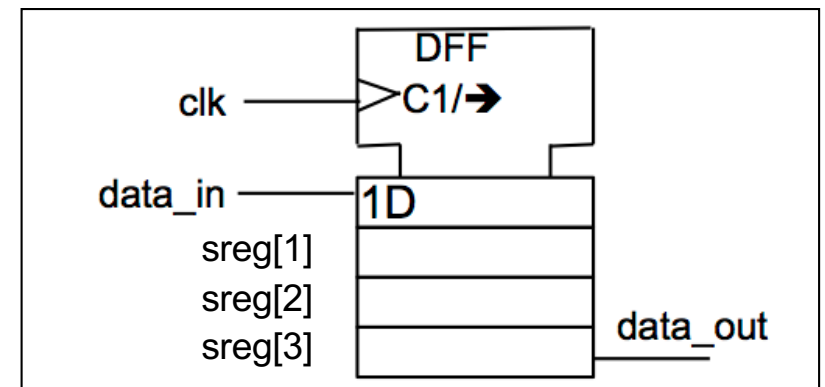

sreg <= {sreg[3:1], data_in};

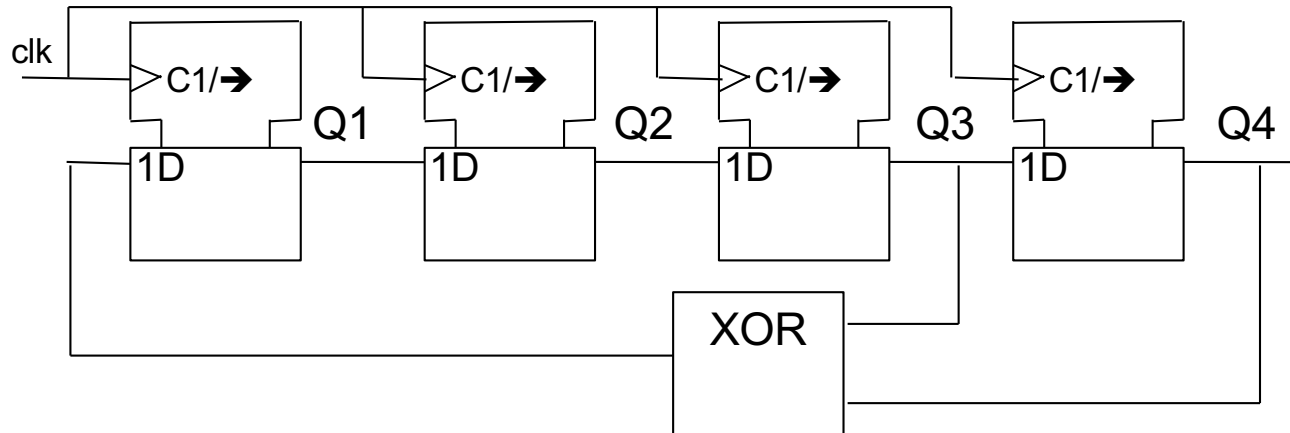
Linear Feedback Shift Register (LFSR) (1)



- ◆ Assuming that the initial value is 4'b0001.
- ◆ This shift register counts through the sequence as shown in the table here.
- ◆ This is now acting as a 4-bit counter, whose count value appears somewhat random.
- ◆ This type of shift register circuit is called “**Linear Feedback Shift Register**” or LFSR.
- ◆ Its value is sort of random, but repeat every $2^N - 1$ cycles (where N = no of bits).
- ◆ The “taps” from the shift register feeding the XOR gate(s) is defined by a polynomial as shown above.

Q4	Q3	Q2	Q1	count
0	0	0	1	1
0	0	1	0	2
0	1	0	0	4
1	0	0	1	9
0	0	1	1	3
0	1	1	0	6
1	1	0	1	13
1	0	1	0	10
0	1	0	1	5
1	0	1	1	11
0	1	1	1	7
1	1	1	1	15
1	1	1	0	14
1	1	0	0	12
1	0	0	0	8
0	0	0	1	1

Primitive Polynomial

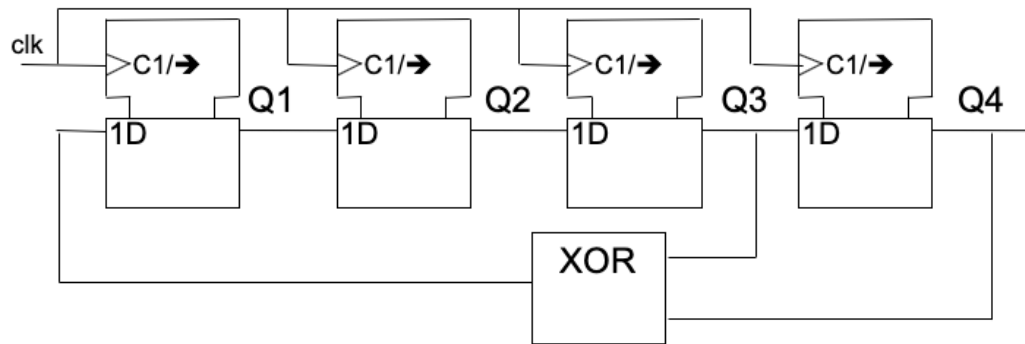


Primitive polynomial: $1 + X^3 + X^4$

- ◆ This circuit implements the LFSR based on this **primitive polynomial**:
- ◆ The polynomial is of order 4 (highest power of x)
- ◆ This produces a **pseudo random binary sequence** (PRBS) of length $2^4 - 1 = 15$
- ◆ Here is a table showing primitive polynomials at different sizes (or orders)


m		m	
3	$1 + X + X^3$	14	$1 + X + X^6 + X^{10} + X^{14}$
4	$1 + X + X^4$	15	$1 + X + X^{15}$
5	$1 + X^2 + X^5$	16	$1 + X + X^3 + X^{12} + X^{16}$
6	$1 + X + X^6$	17	$1 + X^3 + X^{17}$
7	$1 + X^3 + X^7$	18	$1 + X^7 + X^{18}$
8	$1 + X^2 + X^3 + X^4 + X^8$	19	$1 + X + X^2 + X^5 + X^{19}$
9	$1 + X^4 + X^9$	20	$1 + X^3 + X^{20}$
10	$1 + X^3 + X^{10}$	21	$1 + X^2 + X^{21}$
11	$1 + X^2 + X^{11}$	22	$1 + X + X^{22}$
12	$1 + X + X^4 + X^6 + X^{12}$	23	$1 + X^5 + X^{23}$
13	$1 + X + X^3 + X^4 + X^{13}$	24	$1 + X + X^2 + X^7 + X^{24}$

lfsr4.sv

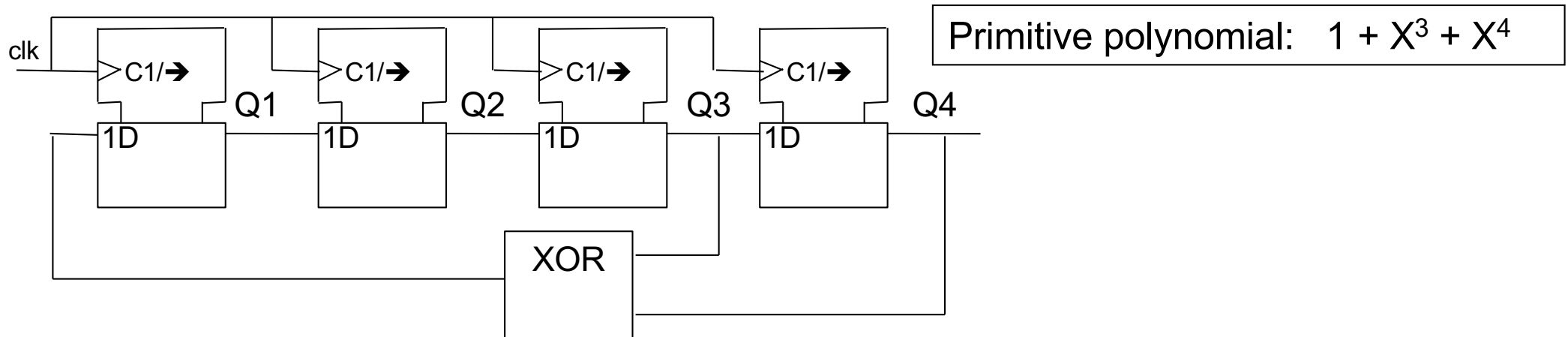


```
module lfsr4 (  
    input logic      clk,      // clock  
    input logic      rst,      // reset  
    output logic [4:1] data_out // pseudo-random output  
);  
  
always_ff @ (posedge clk, posedge rst)  
    if (rst)  
        sreg <= 4'b1;  
    else  
        sreg <= {sreg[3:1], sreg[4] ^ sreg[3]};  
  
assign data_out = sreg;  
endmodule
```

Simplified 4 x 4 ROM array

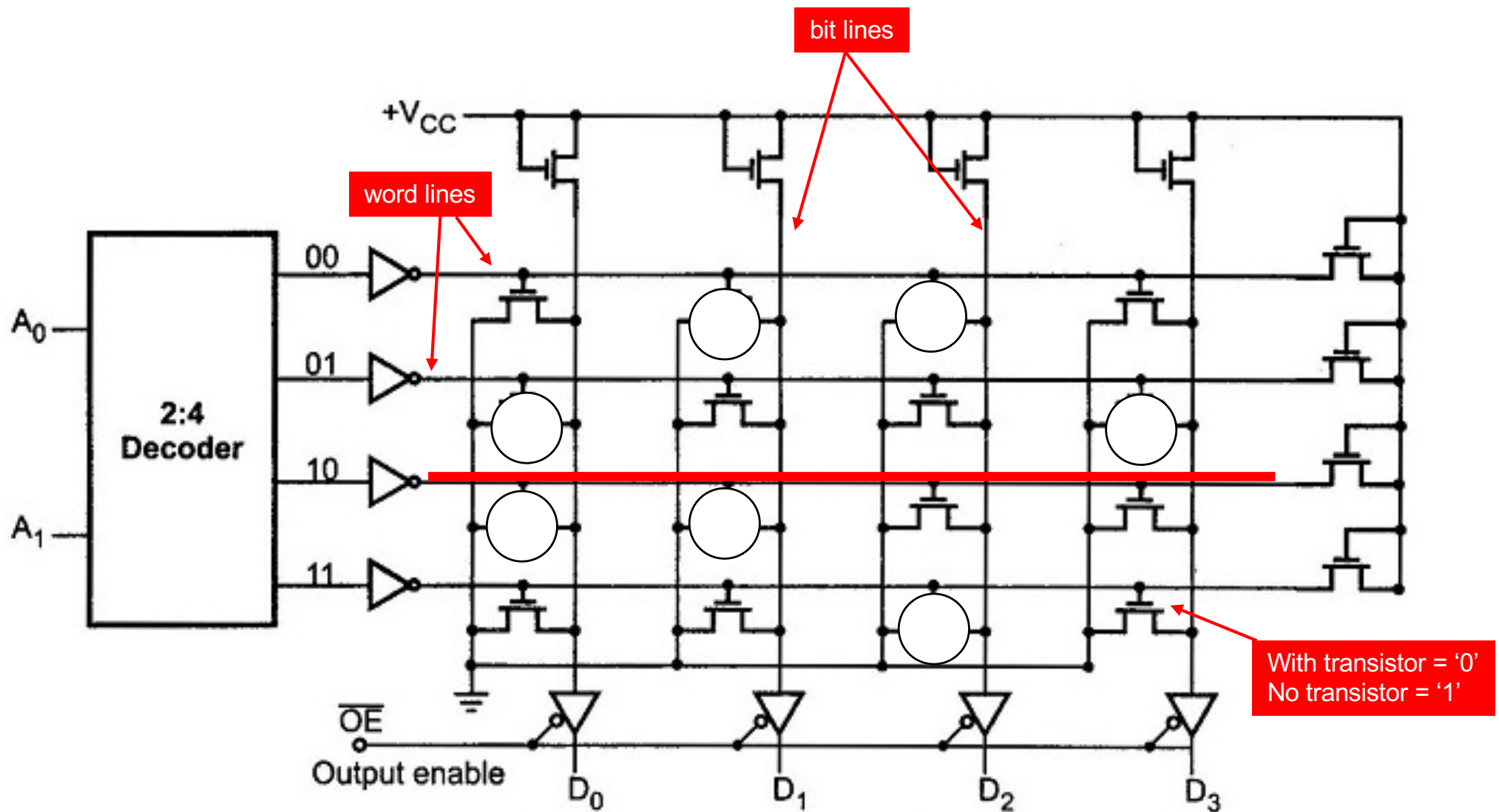


Simplified 8 x 6 Static RAM array

 

System Verilog specification of 256 x 8 ROM


```
1  module rom #(
2      parameter    ADDRESS_WIDTH = 8,
3      parameter    DATA_WIDTH = 8
4  ) (
5      input logic    clk,
6      input logic    [ADDRESS_WIDTH-1:0] addr,
7      output logic    [DATA_WIDTH-1:0] dout
8  );
9
10 logic [DATA_WIDTH-1:0] rom_array [2**ADDRESS_WIDTH-1:0];
11
12 initial begin
13     $display("Loading rom.");
14     $readmemh("sinerom.mem", rom_array);
15 end;
16
17 always_ff @(posedge clk)
18     // output is synchronous
19     dout <= rom_array [addr];
20
21 endmodule
```

 Verilator gives a warning unless you add an extra line!!!!



Initialization of the ROM
 
```
12 initial begin
13     $display("Loading rom.");
14     $readmemh("sinerom.mem", rom_array);
15 end;
```




sinegen.py

```
1 import math
2 import string
3 f = open("sinerom.mem", "w")
4 for i in range(256):
5     v = int(math.cos(2*3.1416*i/256)*127+127)
6     if (i+1)%16 == 0:
7         s = "{hex:2X}\n"
8     else:
9         s = "{hex:2X} "
10    f.write(s.format(hex=v))
11
12 f.close()
```

sinerom.mem

1	FE	FD	FD	FD	FD	FD	FC	FC	FB	FA	FA	F9	F8	F7	F6	F5
2	F4	F3	F1	F0	EF	ED	EB	EA	E8	E6	E5	E3	E1	DF	DD	DA
3	D8	D6	D4	D1	CF	CD	CA	C8	C5	C2	C0	BD	BA	B8	B5	B2
4	AF	AC	A9	A6	A3	A0	9D	9A	97	94	91	8E	8B	88	85	82
5	7E	7B	78	75	72	6F	6C	69	66	63	60	5D	5A	57	54	51
6	4E	4B	48	45	43	40	3D	3B	38	35	33	30	2E	2C	29	27
7	25	23	20	1E	1C	1A	18	17	15	13	12	10	E	D	C	A
8	9	8	7	6	5	4	3	3	2	1	1	0	0	0	0	0
9	0	0	0	0	0	0	1	1	2	3	3	4	5	6	7	8
10	9	A	C	D	E	10	12	13	15	17	18	1A	1C	1E	20	23
11	25	27	29	2C	2E	30	33	35	38	3B	3D	40	43	45	48	4B
12	4E	51	54	57	5A	5D	60	63	66	69	6C	6F	72	75	78	7B
13	7F	82	85	88	8B	8E	91	94	97	9A	9D	A0	A3	A6	A9	AC
14	AF	B2	B5	B8	BA	BD	C0	C2	C5	C8	CA	CD	CF	D1	D4	D6
15	D8	DA	DD	DF	E1	E3	E5	E6	E8	EA	EB	ED	EF	F0	F1	F3
16	F4	F5	F6	F7	F8	F9	FA	FA	FB	FC	FC	FD	FD	FD	FD	FD

Simple Sinewave Generator

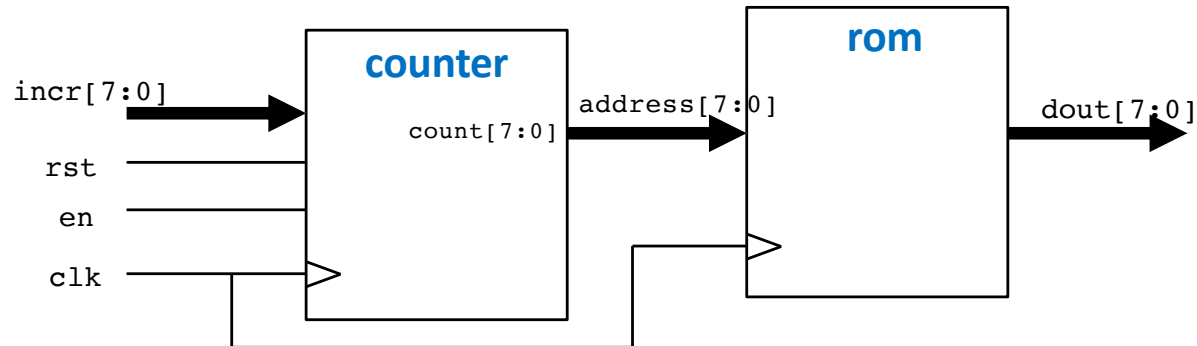

```
1 module sinegen #(
2     parameter A_WIDTH = 8,
3     parameter D_WIDTH = 8
4 )
5 // interface signals
6 input logic clk, // clock
7 input logic rst, // reset
8 input logic en, // enable
9 input logic [D_WIDTH-1:0] incr, // increment for addr counter
10 output logic [D_WIDTH-1:0] dout // output data
11 );
12
13 logic [A_WIDTH-1:0] address; // interconnect wire
14
15 counter addrCounter (
16     .clk (clk),
17     .rst (rst),
18     .en (en),
19     .incr (incr),
20     .count (address)
21 );
22
23 rom sineRom (
24     .clk (clk),
25     .addr (address),
26     .dout (dout)
27 );
28
29 endmodule
```


Instantiate counter module called addrCounter

external signal name

Internal signal name

Parameterised ROM:


```
1  module rom #(
2      parameter    ADDRESS_WIDTH = 8,
3      parameter    DATA_WIDTH = 8
4  ) (
5      input logic    clk,
6      input logic    [ADDRESS_WIDTH-1:0] addr,
7      output logic    [DATA_WIDTH-1:0] dout
8  );
9
10 logic [DATA_WIDTH-1:0] rom_array [2**ADDRESS_WIDTH-1:0];
11
12 initial begin
13     $display("Loading rom.");
14     $readmemh("sinerom.mem", rom_array);
15 end;
16
17 always_ff @(posedge clk)
18     // output is synchronous
19     dout <= rom_array [addr];
20
21 endmodule
22
```

 

```
rom #(10, 9) sineRom_1024x9 (.....)
```

Dual-port ROM

```
1 module rom2ports #(
2     parameter    ADDRESS_WIDTH = 8,
3     parameter    DATA_WIDTH = 8
4 )
5     input logic    clk,
6     input logic    [ADDRESS_WIDTH-1:0]    addr1,
7     input logic    [ADDRESS_WIDTH-1:0]    addr2,
8     output logic    [DATA_WIDTH-1:0]    dout1,
9     output logic    [DATA_WIDTH-1:0]    dout2
10 );
11
12 logic [DATA_WIDTH-1:0] rom_array [2**ADDRESS_WIDTH-1:0];
13
14 initial begin
15     $display("Loading rom.");
16     $readmemh("sinerom.mem", rom_array);
17 end;
18
19 always_ff @(posedge clk) begin
20     // output is synchronous
21     dout1 <= rom_array [addr1];
22     dout2 <= rom_array [addr2];
23 end
24
25 endmodule
```

 

Dual-port RAM

```
1 module ram2ports #(
2     parameter    ADDRESS_WIDTH = 8,
3     parameter    DATA_WIDTH = 8
4 )
5     input logic    clk,
6     input logic    wr_en,
7     input logic    rd_en,
8     input logic [ADDRESS_WIDTH-1:0] wr_addr,
9     input logic [ADDRESS_WIDTH-1:0] rd_addr,
10    input logic [DATA_WIDTH-1:0] din,
11    output logic [DATA_WIDTH-1:0] dout
12 );
13
14 logic [DATA_WIDTH-1:0] ram_array [2**ADDRESS_WIDTH-1:0];
15
16 always_ff @(posedge clk) begin
17     if (wr_en == 1'b1)
18         ram_array[wr_addr] <= din;
19     if (rd_en == 1'b1)
20         // output is synchronous
21         dout <= ram_array [rd_addr];
22 end
23 endmodule
```

